

NAME: SHIVANSH SETHI Univ. Rollno: 2101206 Page no: 1  
COURSE: MCA Sem: 1 Sec: A Student Id: 21711028 , class Roll: 24  
Subject Name: Computer Org & Arch. Subject Code: TMC102 Date: 22/3/22


## Q1    NAND GATE

A NAND Gate is a logic gate that produces a low output i.e 0 only if all its inputs are TRUE, and high output i.e 1 only if it otherwise.

NAND Gate is the inverse of AND Gate. Its circuit is produced by connecting an AND Gate to a NOT Gate.

The NAND gate performs logical NAND operation. It is known as universal gate.

### Circuit Diagram

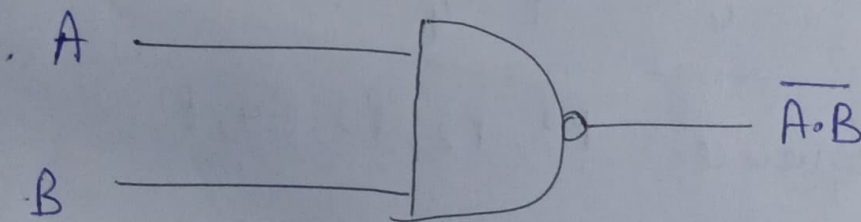

*Shiv*

NAND gate is a "NOT AND Gate".

The output of NAND gate is sense of AND gate.

The output of NAND gate is only logical 0 when and only when all inputs of the gate are 1 and in all other cases the output is high.

Truth Table

Input		Output
A	B	$X = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

*B. S. S. S.*