

Name - Gaurav Awasthi

Course - MCA

University Roll No - 2101070

Student ID - 2171105

Subject Name - Computer Organization

Subject Code - PMC (102)

Date - 22/3/22

Section - B


Ans 1

NAND - A Nand gate ("not AND gate") is a logic gate that produces

a low output (0) only if all its inputs are true, and high output (1) otherwise.

Hence the NAND gate is the inverse of an AND gate, and its circuit is produced by connecting an AND gate to a NOT gate.

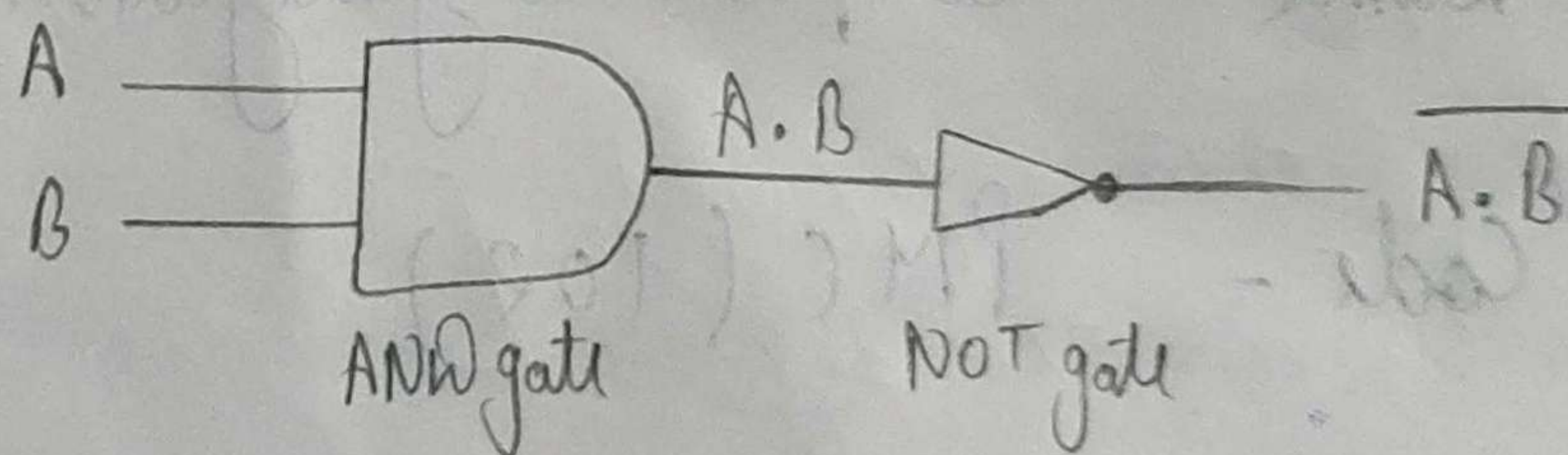The basic logical construction of the NAND gate is shown below (you can see it is an AND gate followed by a NOT gate).



Truth table

Inputs		output
A	B	$X = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0