


Shubham Dhondiyal
Section B

1.

The NAND Gate is a combination of a digital logic AND Gate and a NOT Gate connected together in series.

The NAND gate has an output that is normally a logic level '1' and only goes "Low" to logic level "0" when all of its inputs are at logic level '1'. The logic NAND Gate is the reverse or Complementary form of the AND gate we have seen previously.

Input Logic NAND Gate

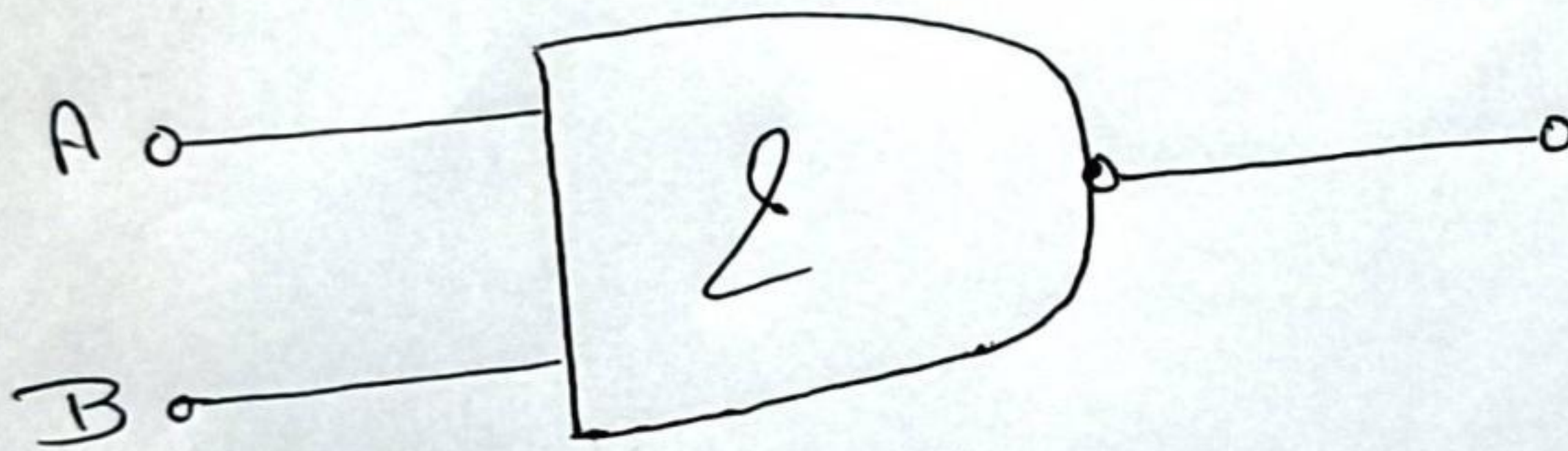

Truth table

<u>B</u>	<u>A</u>	<u>Q</u>
0	0	1
0	1	1
1	0	1
1	1	0

Circuit diagram

