

Name - Taron Kumar Gupta

Date 12/05/2022

Univ Roll no 2101236

Course MCA

Sec A A

Sub - Computer Organisation
& Architecture


Student id - 21711142

Sem - Ist

Ans 1) The NAND gate or "NotAND" gate is the combination of two basic logic gates, the AND gate and the NOT gate connected in series.

The output of a NAND gate is high when either of the inputs is high or if the both inputs are low.

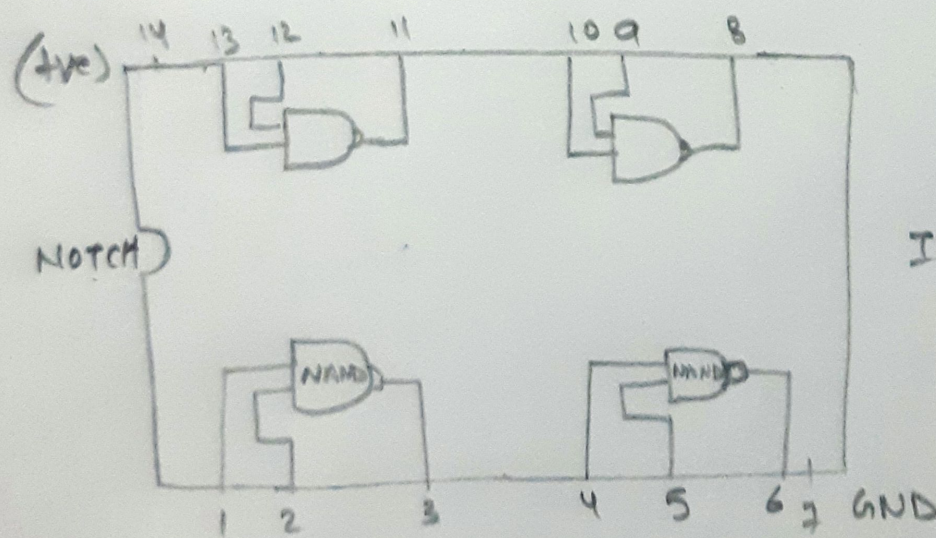The logic NAND function is given by the Boolean expression $Y = \overline{A \cdot B}$. Here A, B are the inputs and Y is the output.



IC NO. 7400

Circuit diagram

Gupta

Truth Table of NAND Gate

Inputs		Output
A	B	$Y = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0