

Name → Shubham Naddiyal

①


Section → B (MCA)

University roll no → 2101215


Student ID → 21711014

NAND → The logic NAND gate is generally called as a "UNIVERSAL GATE", because it is ~~is~~ one of the most used logic gate types all gates can be implemented by NAND gate. Boolean Expression  $Q = \overline{A \cdot B}$ . The NAND gate has an output low (0) only when all input are high (1). It is inverter of AND.

Logic Diagram →

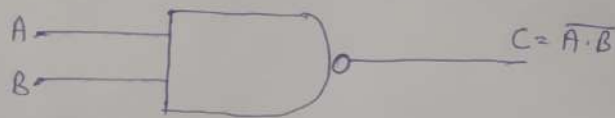

IC diagram  
(+ve)

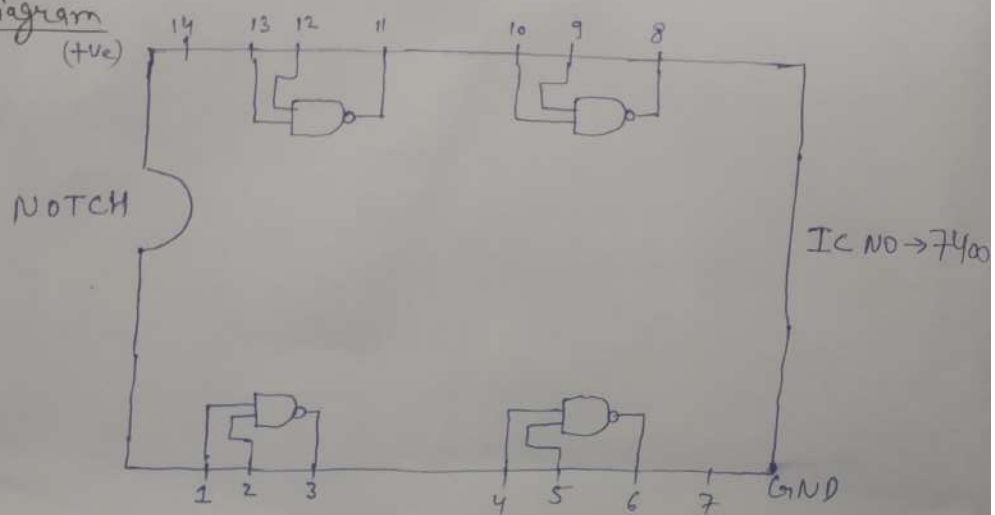

Truth table

Input		output
A	B	$C = \overline{A \cdot B}$
0	0	1
1	0	1
0	1	1
1	1	0

Precaution → All the connection should be proper accordingly to the Circuit diagram.

① Small switch off the power supply immediately.

②

Result → The result of the Experiment has been verified successfully.