

Name \rightarrow Anirudh Botlagura
Course \rightarrow MCA
Section \rightarrow B

Roll no \rightarrow 2101026
Date \rightarrow 22 March 2022
Exam \rightarrow CO Practical

Q1

NAND Gate


The NAND gate is the universal gate, it means all the basic gates such as AND, OR and NOT gate can be constructed using NAND gate.

It is combination of NOT & AND gate, the output state of the NAND gate will be low only when all the inputs are high.

The logic or Boolean expression for the NAND gate is the complement of logical multiplication of inputs denoted by a dot

$$(A \cdot B)' = Y$$

- The 2 input NAND gate.

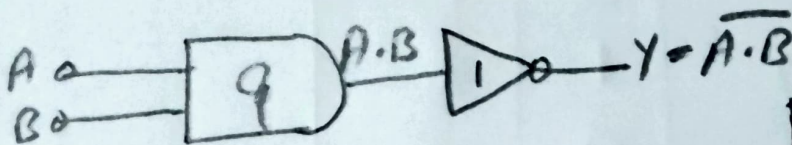


There are $2^2 = 4$ possible combinations of I/P.

Truth Table

Input		OP
A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

3 Input NAND

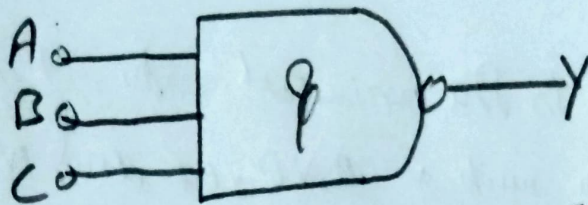There will be $2^3 = 8$ possible combinations of I/P



3-I/P NAND gate

Truth Table

Input			output
A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0