

Name- Anurag Rawat


Univ. Roll no. 2101033

Student ID- 21711266

Course- MCA 10


Subject- Computer Organization and Architecture
PMC-102

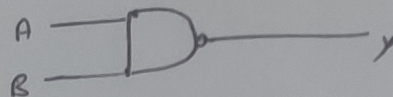
① NAND Gate :- A NOT-AND operation is known as NAND operation. It has n input ($n \geq 2$) and one output.



A	B	\overline{AB}
0	0	1
0	1	1
1	0	1
1	1	0

Truth table

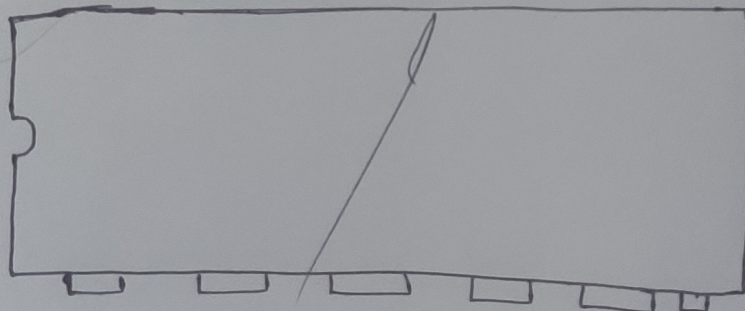

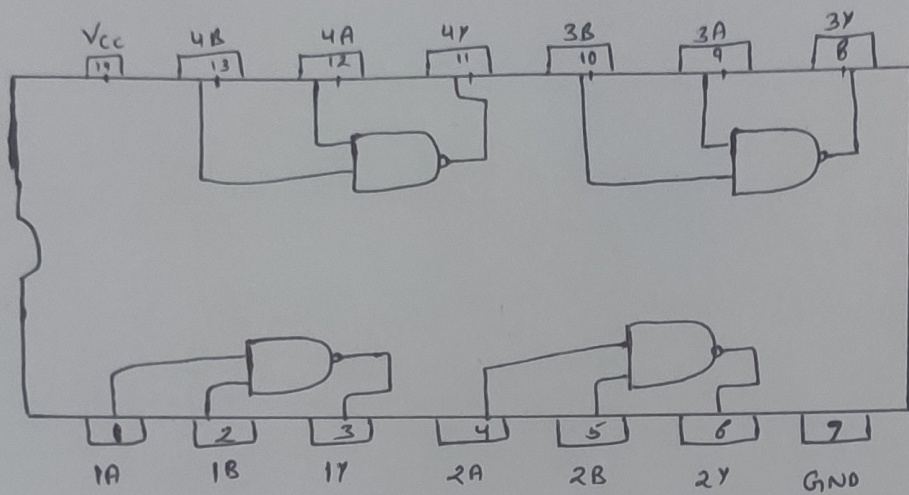

Circuit diagram