

Name - Paras Pawar
Course - MCA A 1st

University
Roll no - 2101141
Roll no - 20


Std - 2171117

Nor gate - It is a universal gate. It is a combination of NOT-OR gate. The output is high only when, all the input are low.

The logical or Boolean expression for the NOR gate is the complement of logical multiplication of input denoted by the plus sign as

$$(A+B)' = Y$$

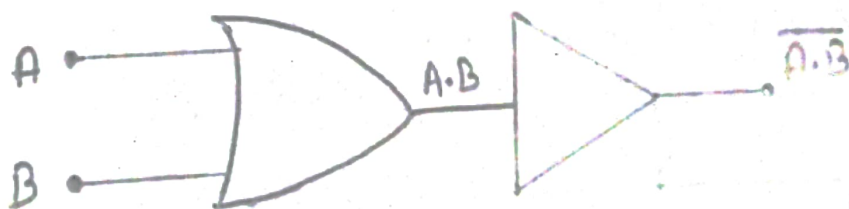The value 'Y' will be true when all of its inputs are set to 0.




NOR

here

Input			Output
A	B	$A \cdot B$	$Y = \overline{A \cdot B}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0


Name - Paras Pawar
Course - mca A 3rd

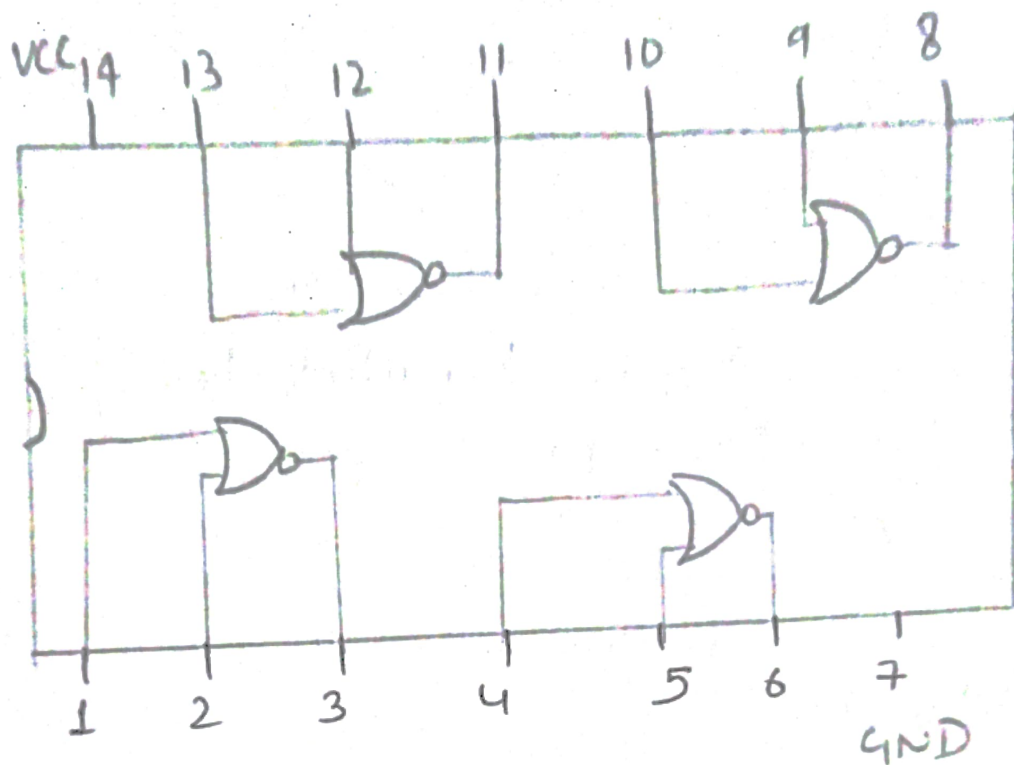University
Roll no - 2101191
Roll no - 20



IC-7402 NOR GATE

$C = 150$

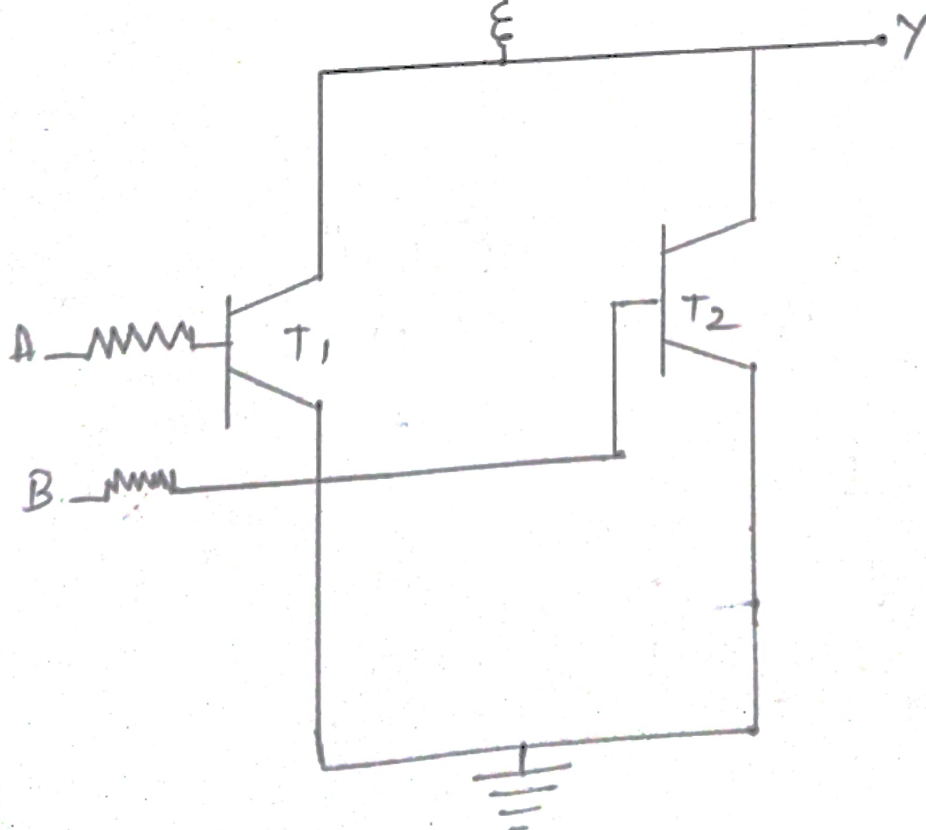

Circuit Diagram

Paras