

Graphic Era Hill University

Wacharam

Name - Rahul Singh Shahi
University Roll No - 2101159

Student ID - 21711172

Date - 22/3/22

Course - MCA

Sem - 1st

Section - B

Subject Name - Computer organization and architecture

Subject Code - PMC(102)



Ans 1

NAND - A Nand gate ("not AND gate") is a logic gate that produces

a low output (0) only if all its input are true, and high output (1) otherwise.

Hence the NAND gate is the inverse of an AND gate, and its circuit is produced by connecting an AND gate to a NOT gate.

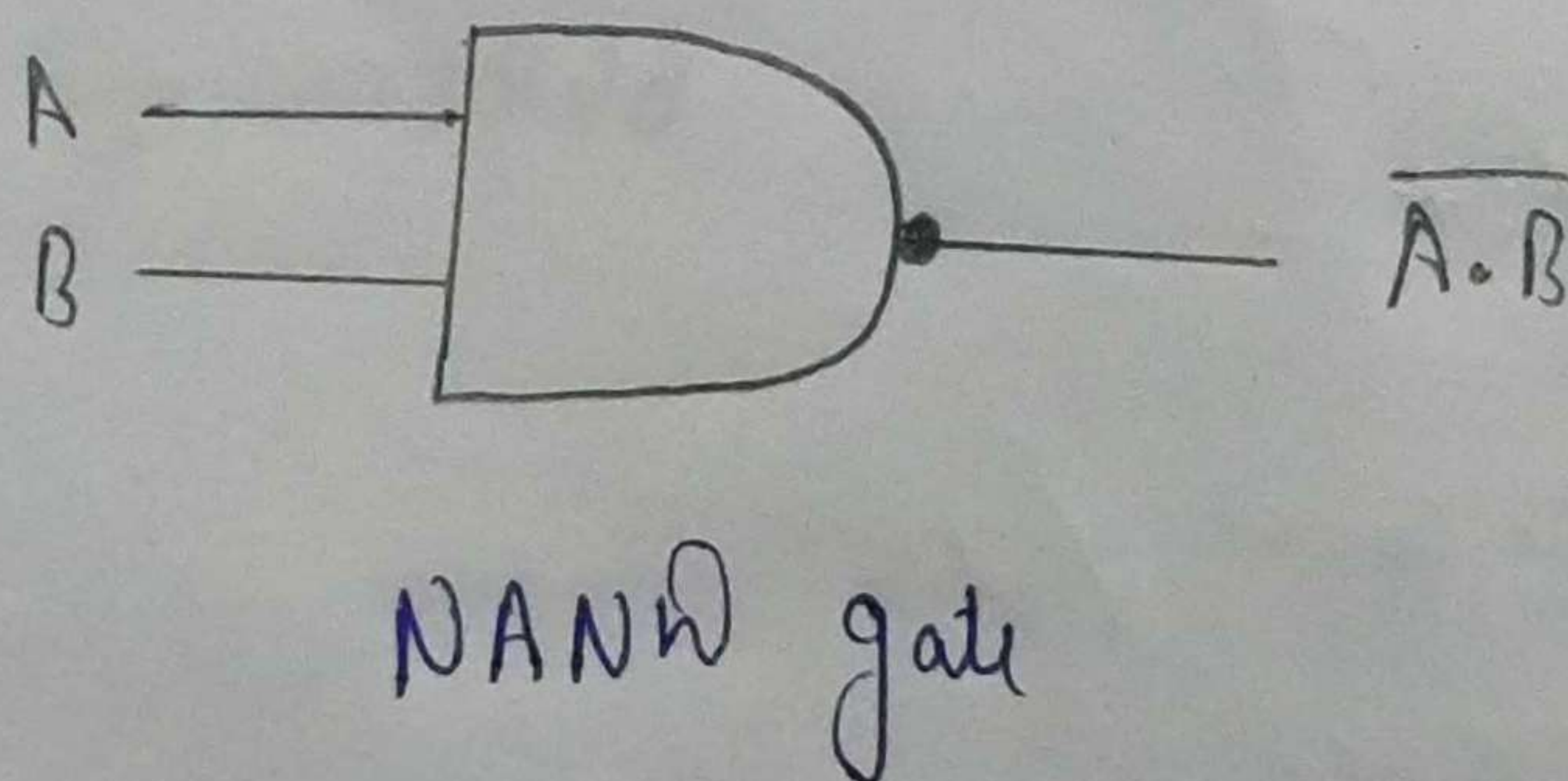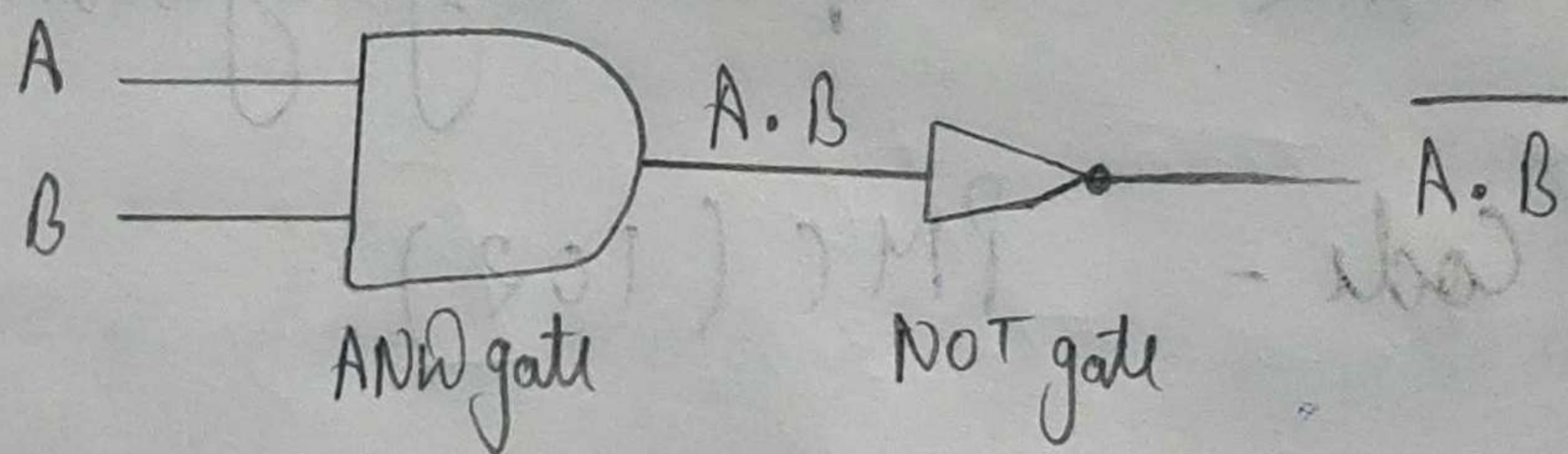The basic logical construction of the NAND gate is shown below (you can see it is an AND gate followed by a NOT gate)



Truth table

Inputs		output
A	B	$X = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0