

NAME \rightarrow MANSI UNIYAL

①

UNIV. ROLLNO \rightarrow 2101115

STUDENT ID \rightarrow 21712134

COURSE \rightarrow MCA(1) SEC \rightarrow B

ENROLL NO. \rightarrow PV-18210082



Ans 1. NAND gate is AND gate succeeded by NOT gate. A NAND gate constitutes one or more inputs with single output. NAND gate has an output that is normally at logic high and only goes to logic low when all its inputs are at logic high.

Its Boolean Expression for NAND Gate $\Rightarrow (A \cdot B)' = Y$

2 Input NAND Gate

In this NAND gate there are only two input values and an output value.

Logic Design -

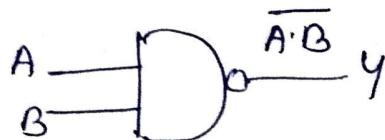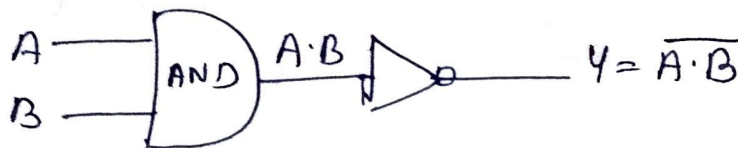

Mansi


Truth table -

(2)

Input		Output
A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

When value of A and B is 0 then $A \cdot B = 0$ and $\overline{A \cdot B} = 1$
When value of A is 0 and B is 1 then $A \cdot B = 0$ and $\overline{A \cdot B} = 1$
When value of A is 1 and B is 0 then $A \cdot B = 0$ and $\overline{A \cdot B} = 1$
When value of A is 1 and B is 1 then $A \cdot B = 1$ and $\overline{A \cdot B} = 0$

Circuit diagram -

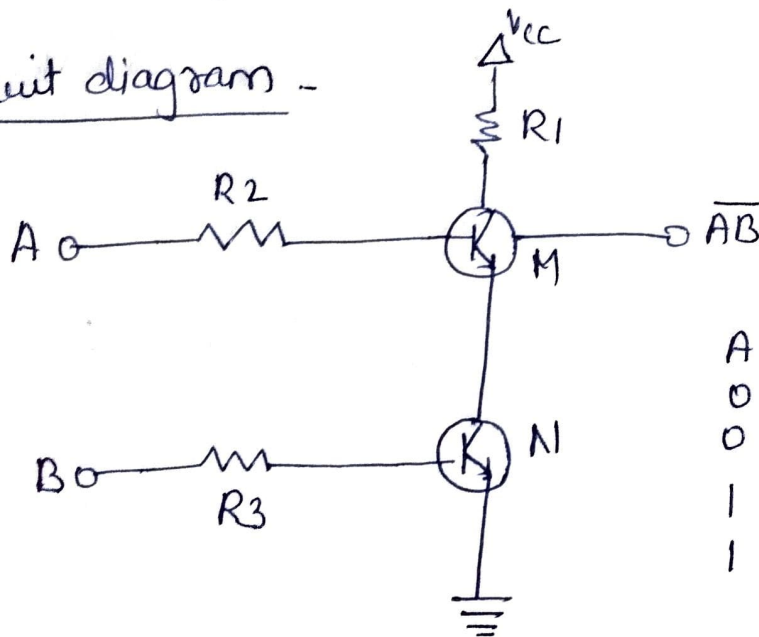

A	B	M	N	Output
0	0	0	0	1
0	1	0	1	1
1	0	1	0	1
1	1	1	1	0

3 Input NAND Gate

3 Input NAND Gate has 3 inputs and 1 output

Logic Design -




Yours

Boolean Expression $\rightarrow (A \cdot B \cdot C)' = Y$

3

Circuit diagram -

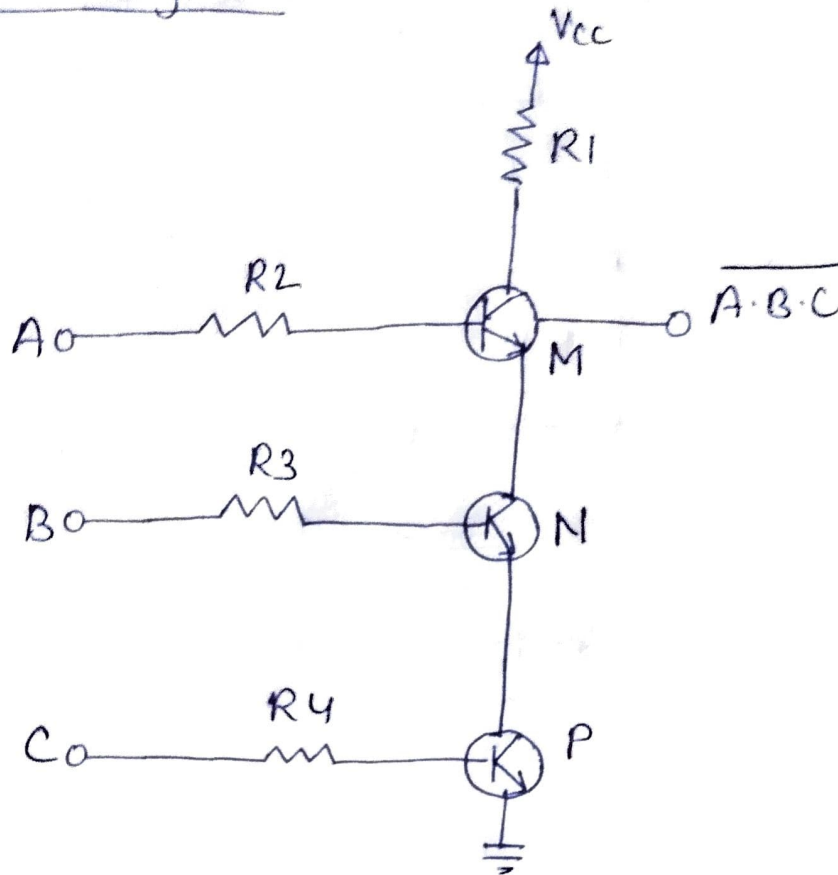

Truth Table -

A	B	C	M	N	P	Output
0	0	0	0	0	0	1
0	0	1	0	0	1	1
0	1	0	0	1	0	1
0	1	1	0	1	1	1
1	0	0	1	0	0	1
1	0	1	1	0	1	1
1	1	0	1	1	0	1
1	1	1	1	1	1	0

flam

When value of A, B, C is 0 then $A \cdot B \cdot C = 0$ and $\overline{A \cdot B \cdot C} = 1$ (1)

When value of $A=0, B=0$ and $C=1$ $A \cdot B \cdot C = 0$ and $\overline{A \cdot B \cdot C} = 1$

When value of $A=0, B=1, C=0 \Rightarrow A \cdot B \cdot C = 0 \Rightarrow \overline{A \cdot B \cdot C} = 1$

$$A=0 \quad B=1 \quad C=1 \quad A \cdot B \cdot C = 0 \quad \overline{A \cdot B \cdot C} = 1$$


$$A=1 \quad B=0 \quad C=0 \quad A \cdot B \cdot C = 0 \quad \overline{A \cdot B \cdot C} = 1$$

$$A=1 \quad B=0 \quad C=1 \quad A \cdot B \cdot C = 0 \quad \overline{A \cdot B \cdot C} = 1$$



$$A=1 \quad B=1 \quad C=0 \quad A \cdot B \cdot C = 0 \quad \overline{A \cdot B \cdot C} = 1$$

$$A=1 \quad B=1 \quad C=1 \quad A \cdot B \cdot C = 1 \quad \overline{A \cdot B \cdot C} = 0$$


AND using NAND

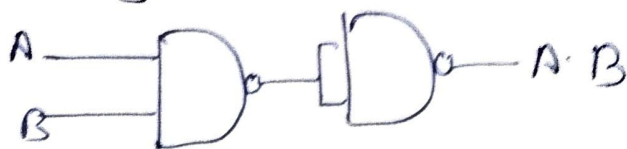


OR using NAND

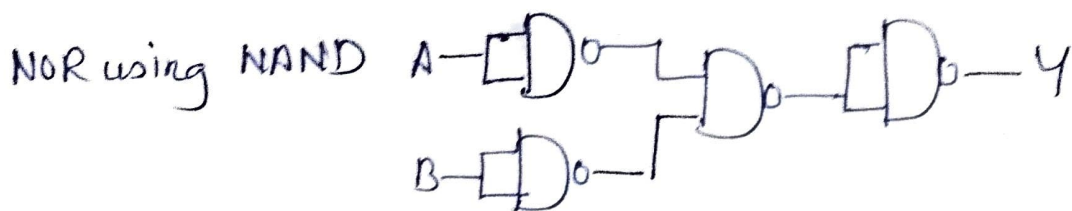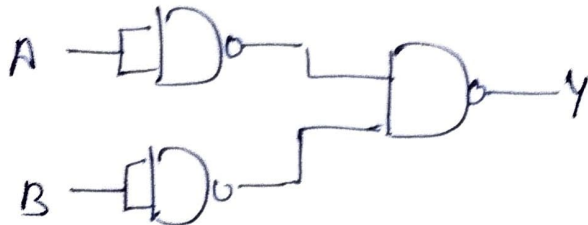

EX-OR using NAND

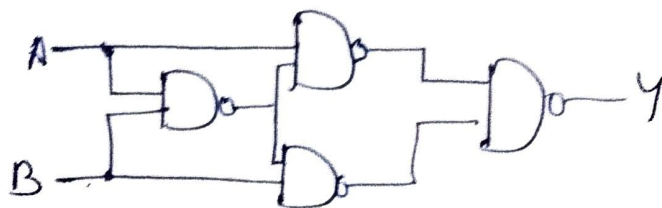

EX-NOR using NAND

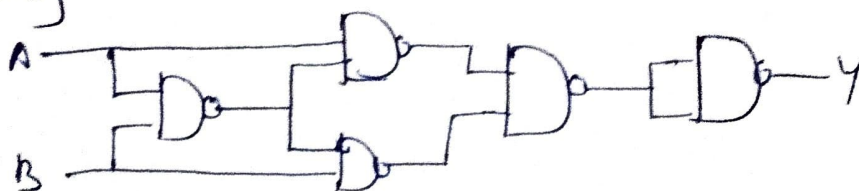

Min